

Electrical Circuit Theory and Technology

Sixth edition

John Bird

Contents

Preface	xii	3.8 Electrical power and energy	54
		3.9 Summary of terms, units and their symbols	55
Part 1 Revision of some basic mathematics	1	4 An introduction to electric circuits	56
1 Some mathematics revision	3	4.1 Standard symbols for electrical components	57
1.1 Use of calculator and evaluating formulae	4	4.2 Electric current and quantity of electricity	57
1.2 Fractions	7	4.3 Potential difference and resistance	58
1.3 Percentages	8	4.4 Basic electrical measuring instruments	58
1.4 Ratio and proportion	10	4.5 Linear and non-linear devices	59
1.5 Laws of indices	13	4.6 Ohm's law	59
1.6 Brackets	16	4.7 Multiples and sub-multiples	59
1.7 Solving simple equations	16	4.8 Conductors and insulators	61
1.8 Transposing formulae	19	4.9 Electrical power and energy	61
1.9 Solving simultaneous equations	21	4.10 Main effects of electric current	64
2 Further mathematics revision	23	4.11 Fuses	64
2.1 Radians and degrees	24	4.12 Insulation and the dangers of constant high current flow	64
2.2 Measurement of angles	25	5 Resistance variation	65
2.3 Trigonometry revision	26	5.1 Resistor construction	66
2.4 Logarithms and exponentials	28	5.2 Resistance and resistivity	66
2.5 Straight line graphs	33	5.3 Temperature coefficient of resistance	68
2.6 Gradients, intercepts and equation of a graph	35	5.4 Resistor colour coding and ohmic values	70
2.7 Practical straight line graphs	37	6 Batteries and alternative sources of energy	73
2.8 Calculating areas of common shapes	38	6.1 Introduction to batteries	74
		6.2 Some chemical effects of electricity	74
		6.3 The simple cell	75
		6.4 Corrosion	76
		6.5 E.m.f. and internal resistance of a cell	76
		6.6 Primary cells	78
		6.7 Secondary cells	79
		6.8 Lithium-ion batteries	81
		6.9 Cell capacity	84
		6.10 Safe disposal of batteries	84
		6.11 Fuel cells	84
		6.12 Alternative and renewable energy sources	85
		6.13 Solar energy	86
		Revision Test 1	89
Main formulae for Part 1 Revision of some basic mathematics	44		
Part 2 Basic electrical engineering principles	47		
3 Units associated with basic electrical quantities	49		
3.1 SI units	49		
3.2 Charge	50		
3.3 Force	50		
3.4 Work	51		
3.5 Power	52		
3.6 Electrical potential and e.m.f.	53		
3.7 Resistance and conductance	53		

7 Series and parallel networks	90	11 Electromagnetic induction	145
7.1 Series circuits	91	11.1 Introduction to electromagnetic induction	146
7.2 Potential divider	92	11.2 Laws of electromagnetic induction	147
7.3 Parallel networks	94	11.3 Rotation of a loop in a magnetic field	150
7.4 Current division	96	11.4 Inductance	151
7.5 Loading effect	99	11.5 Inductors	152
7.6 Potentiometers and rheostats	100	11.6 Energy stored	153
7.7 Relative and absolute voltages	103	11.7 Inductance of a coil	153
7.8 Earth potential and short circuits	104	11.8 Mutual inductance	155
7.9 Wiring lamps in series and in parallel	104		
8 Capacitors and capacitance	106	12 Electrical measuring instruments and measurements	158
8.1 Introduction to capacitors	107	12.1 Introduction	159
8.2 Electrostatic field	107	12.2 Analogue instruments	159
8.3 Electric field strength	108	12.3 Shunts and multipliers	159
8.4 Capacitance	108	12.4 Electronic instruments	161
8.5 Capacitors	109	12.5 The ohmmeter	161
8.6 Electric flux density	110	12.6 Multimeters	162
8.7 Permittivity	110	12.7 Wattmeters	162
8.8 The parallel plate capacitor	111	12.8 Instrument 'loading' effect	162
8.9 Capacitors connected in parallel and series	112	12.9 The oscilloscope	164
8.10 Dielectric strength	116	12.10 Virtual test and measuring instruments	169
8.11 Energy stored	117	12.11 Virtual digital storage oscilloscopes	170
8.12 Practical types of capacitor	117	12.12 Waveform harmonics	173
8.13 Supercapacitors	119	12.13 Logarithmic ratios	174
8.14 Discharging capacitors	121	12.14 Null method of measurement	176
		12.15 Wheatstone bridge	177
		12.16 D.c. potentiometer	177
		12.17 A.c. bridges	178
		12.18 Measurement errors	179
9 Magnetic circuits	122	13 Semiconductor diodes	182
9.1 Introduction to magnetism and magnetic circuits	123	13.1 Types of material	183
9.2 Magnetic fields	124	13.2 Semiconductor materials	183
9.3 Magnetic flux and flux density	125	13.3 Conduction in semiconductor materials	185
9.4 Magnetomotive force and magnetic field strength	125	13.4 The p-n junction	185
9.5 Permeability and B - H curves	126	13.5 Forward and reverse bias	186
9.6 Reluctance	127	13.6 Semiconductor diodes	189
9.7 Composite series magnetic circuits	129	13.7 Characteristics and maximum ratings	190
9.8 Comparison between electrical and magnetic quantities	132	13.8 Rectification	190
9.9 Hysteresis and hysteresis loss	132	13.9 Zener diodes	190
		13.10 Silicon controlled rectifiers	192
		13.11 Light emitting diodes	193
		13.12 Varactor diodes	193
		13.13 Schottky diodes	193
Revision Test 2	134	14 Transistors	195
10 Electromagnetism	135	14.1 Transistor classification	196
10.1 Magnetic field due to an electric current	136	14.2 Bipolar junction transistors (BJTs)	196
10.2 Electromagnets	137	14.3 Transistor action	197
10.3 Force on a current-carrying conductor	139	14.4 Leakage current	198
10.4 Principle of operation of a simple d.c. motor	142	14.5 Bias and current flow	199
10.5 Principle of operation of a moving-coil instrument	143	14.6 Transistor operating configurations	199
10.6 Force on a charge	143		

26.5	Multiplication and division using complex numbers in polar form	419	33 Introduction to network analysis	497	
26.6	De Moivre's theorem – powers and roots of complex numbers	420	33.1	Introduction	497
27 Application of complex numbers to series a.c. circuits		423	33.2	Solution of simultaneous equations using determinants	498
27.1	Introduction	423	33.3	Network analysis using Kirchhoff's laws	499
27.2	Series a.c. circuits	424	34 Mesh-current and nodal analysis	507	
27.3	Further worked problems on series a.c. circuits	430	34.1	Mesh-current analysis	507
28 Application of complex numbers to parallel a.c. networks		435	34.2	Nodal analysis	511
28.1	Introduction	435	35 The superposition theorem	518	
28.2	Admittance, conductance and susceptance	436	35.1	Introduction	518
28.3	Parallel a.c. networks	439	35.2	Using the superposition theorem	518
28.4	Further worked problems on parallel a.c. networks	443	35.3	Further worked problems on the superposition theorem	523
29 Power in a.c. circuits		446	36 Thévenin's and Norton's theorems	528	
29.1	Introduction	446	36.1	Introduction	528
29.2	Determination of power in a.c. circuits	447	36.2	Thévenin's theorem	529
29.3	Power triangle and power factor	449	36.3	Further worked problems on Thévenin's theorem	535
29.4	Use of complex numbers for determination of power	450	36.4	Norton's theorem	539
29.5	Power factor improvement	454	36.5	Thévenin and Norton equivalent networks	546
Revision Test 8		459	Revision Test 10	551	
30 A.c. bridges		460	37 Delta–star and star–delta transformations	552	
30.1	Introduction	461	37.1	Introduction	552
30.2	Balance conditions for an a.c. bridge	461	37.2	Delta and star connections	552
30.3	Types of a.c. bridge circuit	462	37.3	Delta–star transformation	553
30.4	Worked problems on a.c. bridges	467	37.4	Star–delta transformation	561
31 Series resonance and Q-factor		471	38 Maximum power transfer theorems and impedance matching	565	
31.1	Introduction	472	38.1	Maximum power transfer theorems	566
31.2	Series resonance	472	38.2	Impedance matching	571
31.3	Q-factor	474	Revision Test 11	574	
31.4	Voltage magnification	476	39 Complex waveforms	575	
31.5	Q-factors in series	478	39.1	Introduction	576
31.6	Bandwidth	479	39.2	The general equation for a complex waveform	576
31.7	Small deviations from the resonant frequency	483	39.3	Harmonic synthesis	577
32 Parallel resonance and Q-factor		486	39.4	Fourier series of periodic and non-periodic functions	585
32.1	Introduction	486	39.5	Even and odd functions and Fourier series over any range	590
32.2	The $LR-C$ parallel network	487	39.6	R.m.s. value, mean value and the form factor of a complex wave	594
32.3	Dynamic resistance	488	39.7	Power associated with complex waves	597
32.4	The $LR-CR$ parallel network	488	39.8	Harmonics in single-phase circuits	599
32.5	Q-factor in a parallel network	489	39.9	Further worked problems on harmonics in single-phase circuits	602
32.6	Further worked problems on parallel resonance and Q-factor	493	39.10	Resonance due to harmonics	606
Revision Test 9		496	39.11	Sources of harmonics	608

40 A numerical method of harmonic analysis	612	Revision Test 13	697
40.1 Introduction	612		
40.2 Harmonic analysis on data given in tabular or graphical form	612		
40.3 Complex waveform considerations	616		
41 Magnetic materials	619	45 Filter networks	698
41.1 Revision of terms and units used with magnetic circuits	620	45.1 Introduction	698
41.2 Magnetic properties of materials	621	45.2 Basic types of filter sections	699
41.3 Hysteresis and hysteresis loss	622	45.3 The characteristic impedance and the attenuation of filter sections	701
41.4 Eddy current loss	626	45.4 Ladder networks	702
41.5 Separation of hysteresis and eddy current losses	629	45.5 Low-pass filter sections	703
41.6 Non-permanent magnetic materials	631	45.6 High-pass filter sections	709
41.7 Permanent magnetic materials	633	45.7 Propagation coefficient and time delay in filter sections	714
		45.8 ' <i>m</i> -derived' filter sections	720
Revision Test 12	634	45.9 Practical composite filters	725
42 Dielectrics and dielectric loss	635	46 Magnetically coupled circuits	728
42.1 Electric fields, capacitance and permittivity	635	46.1 Introduction	728
42.2 Polarization	636	46.2 Self-inductance	728
42.3 Dielectric strength	636	46.3 Mutual inductance	729
42.4 Thermal effects	637	46.4 Coupling coefficient	730
42.5 Mechanical properties	638	46.5 Coils connected in series	731
42.6 Types of practical capacitor	638	46.6 Coupled circuits	734
42.7 Liquid dielectrics and gas insulation	638	46.7 Dot rule for coupled circuits	739
42.8 Dielectric loss and loss angle	638	47 Transmission lines	746
43 Field theory	642	47.1 Introduction	746
43.1 Field plotting by curvilinear squares	643	47.2 Transmission line primary constants	747
43.2 Capacitance between concentric cylinders	646	47.3 Phase delay, wavelength and velocity of propagation	748
43.3 Capacitance of an isolated twin line	651	47.4 Current and voltage relationships	749
43.4 Energy stored in an electric field	654	47.5 Characteristic impedance and propagation coefficient in terms of the primary constants	751
43.5 Induced e.m.f. and inductance	656	47.6 Distortion on transmission lines	755
43.6 Inductance of a concentric cylinder (or coaxial cable)	656	47.7 Wave reflection and the reflection coefficient	757
43.7 Inductance of an isolated twin line	659	47.8 Standing-waves and the standing-wave ratio	760
43.8 Energy stored in an electromagnetic field	662	48 Transients and Laplace transforms	765
44 Attenuators	665	48.1 Introduction	766
44.1 Introduction	666	48.2 Response of <i>R-C</i> series circuit to a step input	766
44.2 Characteristic impedance	666	48.3 Response of <i>R-L</i> series circuit to a step input	768
44.3 Logarithmic ratios	668	48.4 <i>L-R-C</i> series circuit response	771
44.4 Symmetrical T- and π -attenuators	670	48.5 Introduction to Laplace transforms	774
44.5 Insertion loss	675	48.6 Inverse Laplace transforms and the solution of differential equations	779
44.6 Asymmetrical T- and π -sections	678	48.7 Laplace transform analysis directly from the circuit diagram	784
44.7 The L-section attenuator	681		
44.8 Two-port networks in cascade	683		
44.9 <i>ABCD</i> parameters	686		
44.10 <i>ABCD</i> parameters for networks	689		
44.11 Characteristic impedance in terms of <i>ABCD</i> parameters	695		

48.8	<i>L-R-C</i> series circuit using Laplace transforms	794
48.9	Initial conditions	797
Revision Test 14		801
Main formulae for Part 4 Advanced circuit theory and technology		802
Part 5 General reference		807
	Standard electrical quantities – their symbols and units	809
	Greek alphabet	812
	Common prefixes	813
	Resistor colour coding and ohmic values	814
	Answers to Practice Exercises	815
	Index	837

On the Website

Some practical laboratory experiments

1	Ohm's law	2
2	Series-parallel d.c. circuit	3
3	Superposition theorem	4
4	Thévenin's theorem	6
5	Use of a CRO to measure voltage, frequency and phase	8
6	Use of a CRO with a bridge rectifier circuit	9
7	Measurement of the inductance of a coil	10
8	Series a.c. circuit and resonance	11
9	Parallel a.c. circuit and resonance	13
10	Charging and discharging a capacitor	15

To download and edit go to:
www.routledge.com/cw/bird